

# 8. Design Tradeoffs

6.004x Computation Structures  
Part 1 – Digital Circuits


Copyright © 2015 MIT EECS

# Optimizing Your Design

There are a large number of implementations of the same functionality -- each represents a different point in the area-time-power space

## Optimization metrics:

 1. Area of the design
2. Throughput
3. Latency
4. Power consumption
5. Energy of executing a task
6. ...



©Advanced Micro Devices (with permission)


VS.



Justin I4 (CC BY-SA 4.0)

# CMOS Static Power Dissipation

MOSFET

 


- 1 Tunneling current through gate oxide:  $\text{SiO}_2$  is a very good insulator, but when very thin ( $< 20\text{\AA}$ ) electrons can tunnel across.

- 2 Current leakage from drain to source even though MOSFET is “off” (aka sub-threshold conduction)


- Leakage gets larger as difference between  $V_{\text{TH}}$  and “off” gate voltage (eg,  $V_{\text{OL}}$  in an nfet) gets smaller. Significant as  $V_{\text{TH}}$  has become smaller.
- Fix: 3D FINFET wraps gate around inversion region

FINFET

 

Irene Ringworm (CC BY-SA 3.0)

# CMOS Dynamic Power Dissipation

 


Power dissipated to discharge C:

$$\begin{aligned}
 P_{NFET} &= f_{CLK} \int_0^{t_{CLK}/2} i_{NFET} V_{OUT} dt \\
 &= f_{CLK} \int_0^{t_{CLK}/2} -C \frac{dV_{OUT}}{dt} V_{OUT} dt \\
 &= f_{CLK} C \int_{V_{DD}}^0 -V_{OUT} dV_{OUT} \\
 &= f_{CLK} C \frac{V_{DD}^2}{2}
 \end{aligned}$$

Power dissipated to recharge C:

$$\begin{aligned}
 P_{PFET} &= f_{CLK} \int_{t_{CLK}/2}^{t_{CLK}} i_{PFET} V_{OUT} dt \\
 &= f_{CLK} \int_{t_{CLK}/2}^{t_{CLK}} C \frac{dV_{OUT}}{dt} V_{OUT} dt \\
 &= f_{CLK} C \int_0^{V_{DD}} V_{OUT} dV_{OUT} \\
 &= f_{CLK} C \frac{V_{DD}^2}{2}
 \end{aligned}$$

# CMOS Dynamic Power Dissipation

 

Power dissipated

$$= f C V_{DD}^2 \text{ per node}$$

$$= f N C V_{DD}^2 \text{ per chip}$$

where

$f$  = frequency of charge/discharge

$N$  = number of changing nodes/chip

“Back of the envelope”: trends

$f \sim 1\text{GHz} = 1\text{e}9 \text{ cycles/sec}$

$N \sim 1\text{e}8 \text{ changing nodes/cycle}$

$C \sim 1\text{fF} = 1\text{e}-15 \text{ farads/node}$



$V \sim 1\text{V}$

$\Rightarrow 100 \text{ Watts}$



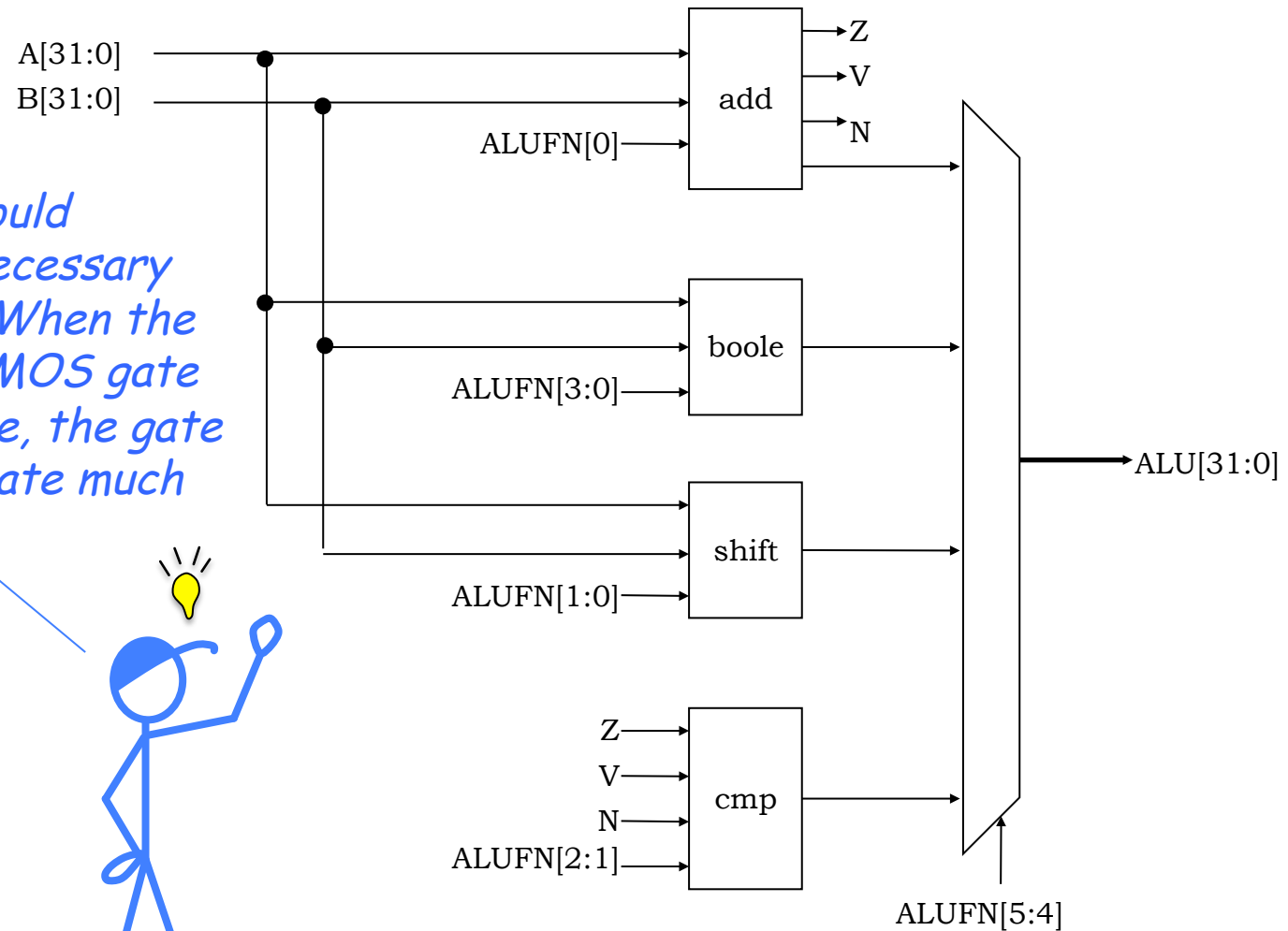 
# How Can We Reduce Power?

*What if we could eliminate unnecessary transitions? When the output of a CMOS gate doesn't change, the gate doesn't dissipate much power!*




# Fewer Transitions → Lower Power

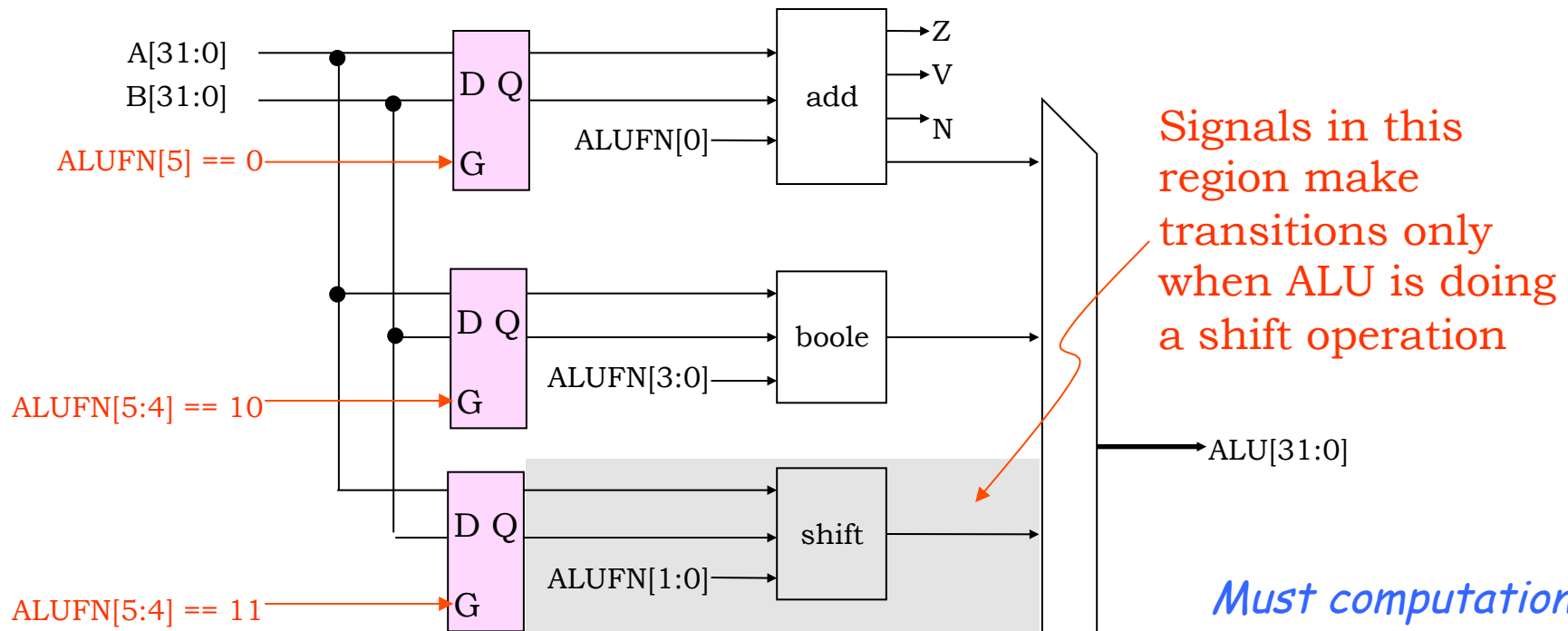

Variations: Dynamically adjust  $t_{\text{CLK}}$  or  $V_{\text{DD}}$  (either overall or in specific regions) to accommodate workload.

 
*Must computation consume energy?  
See §6.5 of Notes*







# Improving Speed: Adder Example

 

Worse-case path: carry propagation from LSB to MSB, e.g., when adding 11...111 to 00...001.

$$t_{PD} = (N-1) * (\underbrace{t_{PD,NAND3} + t_{PD,NAND2}}_{\text{CI to CO}}) + \underbrace{t_{PD,XOR}}_{\text{CI}_{N-1} \text{ to } S_{N-1}} \approx \Theta(N)$$

$\Theta(N)$  is read “order N” and tells us that the latency of our adder grows in proportion to the number of bits in the operands.

# Performance/Cost Analysis


“Order Of” notation:

"g(n) is of order f(n)"  $g(n) = \Theta(f(n))$

$g(n) = \Theta(f(n))$  if there exist  $C_2 \geq C_1 > 0$   
such that for all but finitely many  
integral  $n \geq 0$

$$C_1 \cdot f(n) \leq g(n) \leq C_2 \cdot f(n)$$

 $\Theta(\dots)$  implies both  
inequalities;  
 $O(\dots)$  implies only  
the second.



$g(n) = O(f(n))$


Example:

$$n^2 + 2n + 3 = \Theta(n^2)$$

since

$$n^2 < n^2 + 2n + 3 < 2n^2$$


“almost always”

 
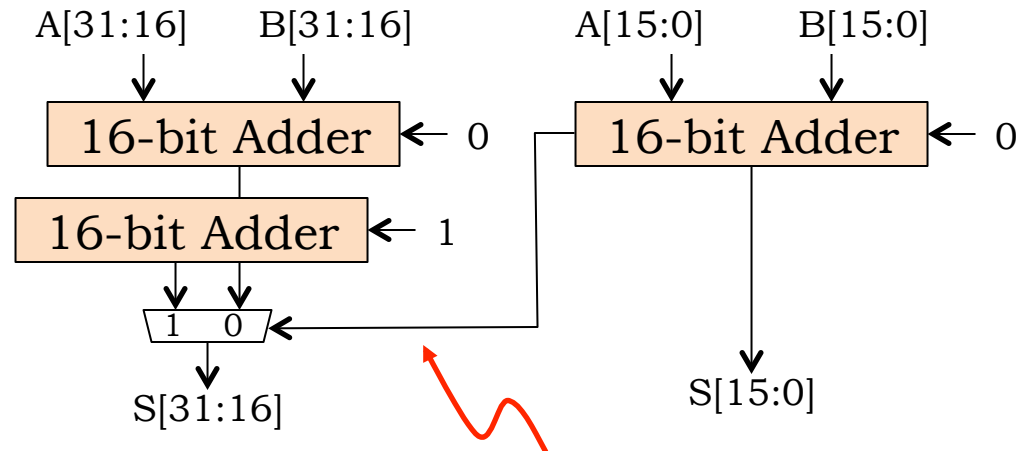
# Carry Select Adders

*Hmm. Can we get the high half of the adder working in parallel with the low half?*

*Two copies of the high half of the adder: one assumes a carry-in of "0", the other carry-in of "1".*



*Once the low half computes the actual value of the carry-in to the high half, use it select the correct version of the high-half addition.*


$$t_{PD} = 16 * t_{PD, CI \rightarrow CO} + t_{PD, MUX2} \approx \text{half of } 32 * t_{PD, CI \rightarrow CO}$$



Aha! Apply the same strategy to build 16-bit adders from 8-bit adders. And 8-bit adders from 4-bit adders, and so on. Resulting  $t_{PD}$  for N-bit adder is  $\Theta(\log N)$ .
 
# 32-bit Carry Select Adder

Practical Carry-select addition: choose block sizes so that trial sums and carry-in from previous stage arrive simultaneously at MUX.





# Wanted: Faster Carry Logic!

Let's see if we can improve the speed by rewriting the equations for  $C_{OUT}$ :

$$C_{OUT} = AB + AC_{IN} + BC_{IN}$$


$$= AB + (A + B)C_{IN}$$

$$= G + P C_{IN} \quad \text{where } G = AB \text{ and } P = A + B$$


$\nearrow$  generate  $\nearrow$  propagate

Actually,  $P$  is usually defined as  $P = A \oplus B$  which won't change  $C_{OUT}$  but will allow us to express  $S$  as a simple function of  $P$  and  $C_{IN}$ :

$$S = P \oplus C_{IN}$$

 

 *CO logic using only  
3 NAND2 gates!  
Think I'll borrow  
that for my FA  
circuit!*




# Carry Look-ahead Adders (CLA)

We can build a hierarchical carry chain by generalizing our definition of the Carry Generate/Propagate (GP) Logic. We start by dividing our addend into two parts, a higher part, H, and a lower part, L. The GP function can be expressed as follows:


$$G_{HL} = G_H + P_H G_L$$

$$P_{HL} = P_H P_L$$

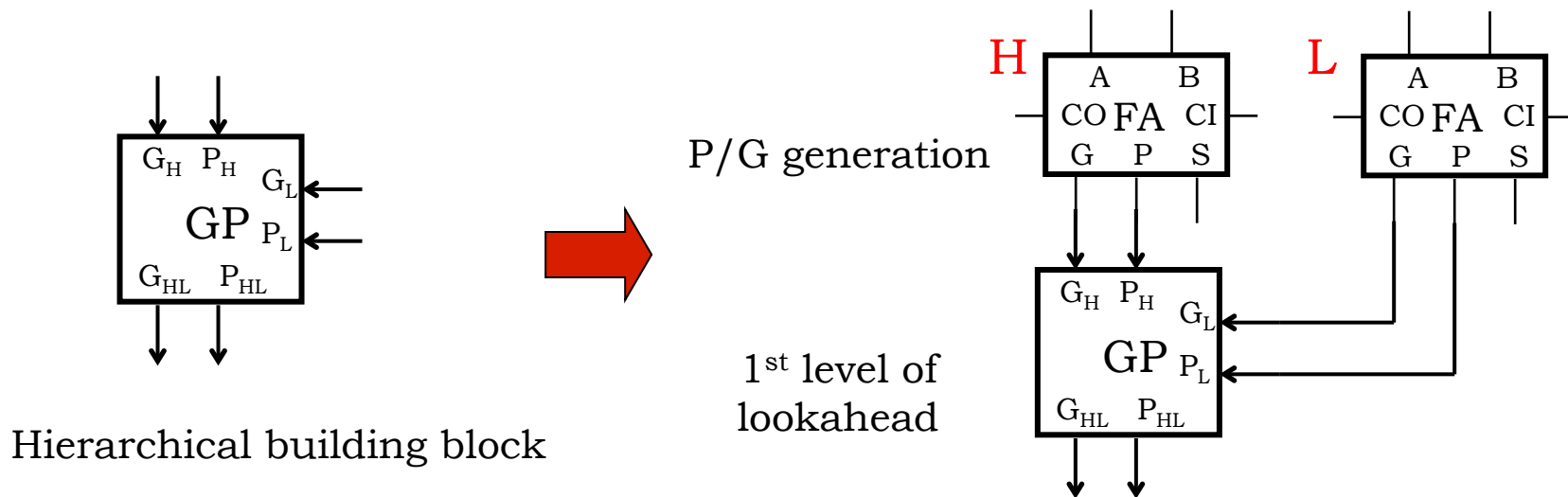Generate a carry out if the high part generates one, or if the low part generates one and the high part propagates it.  
Propagate a carry if both the high and low parts propagate theirs.



# 8-bit CLA (generate G & P)

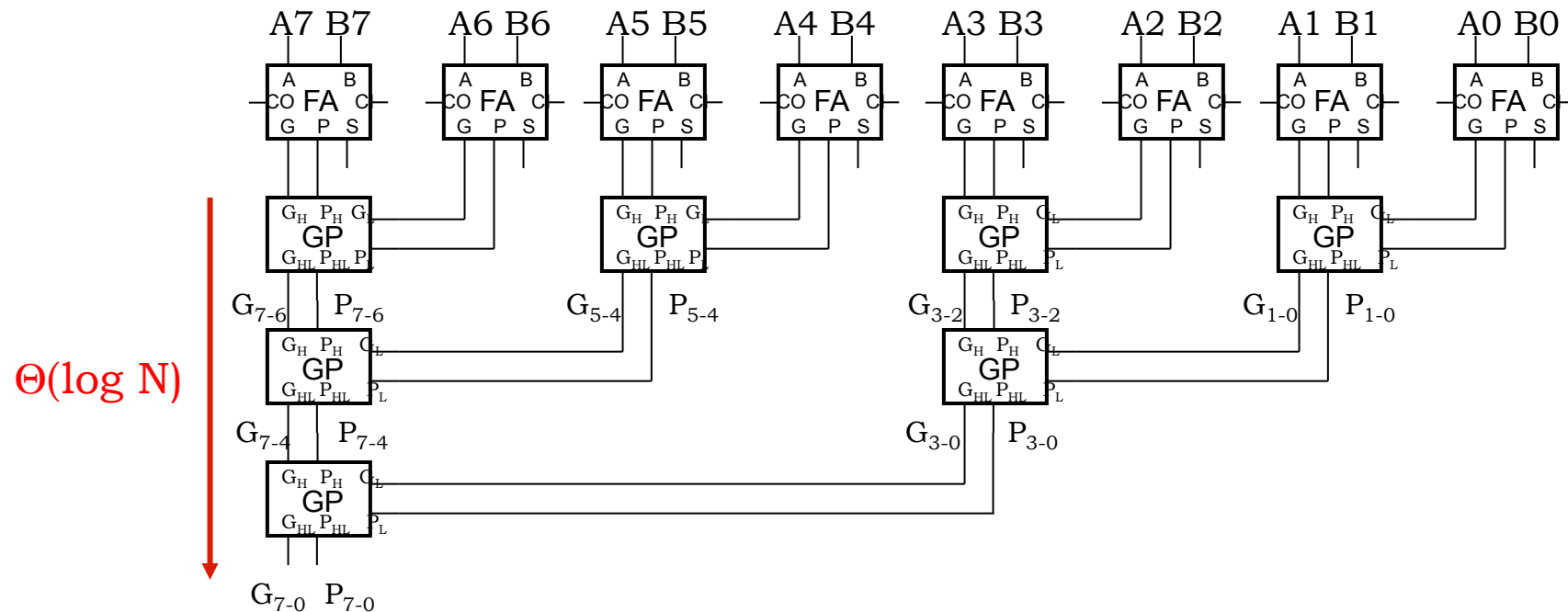

We can build a tree of GP units to compute the generate and propagate logic for any sized adder. Assuming  $N$  is a power of 2, we'll need  $N-1$  GP units.

This will let us to quickly compute the carry-ins for each FA!




# 8-bit CLA (carry generation)


Now, given the value of the carry-in of the least-significant bit, we can generate the carries for every adder.

$$c_H = G_L + P_L c_{in}$$


$$c_L = c_{in}$$

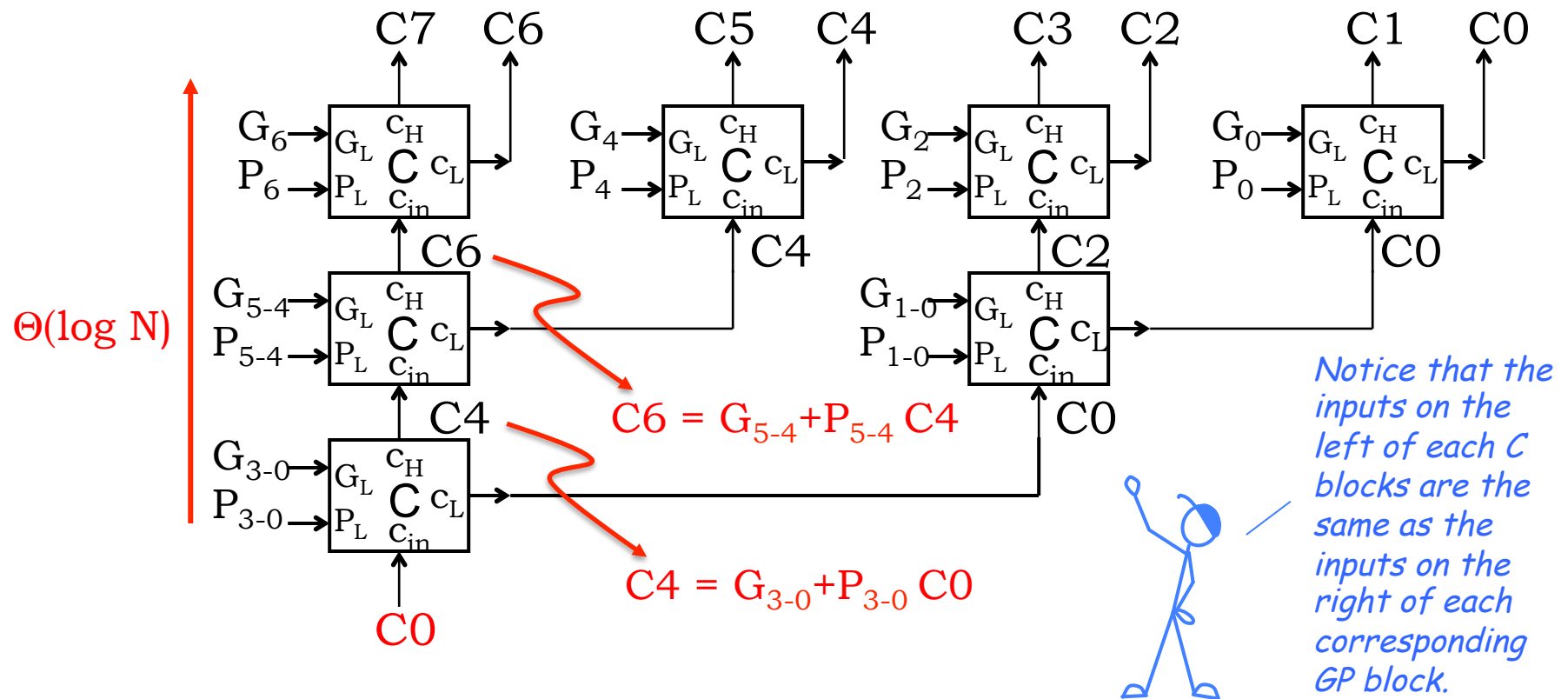

# 8-bit CLA (complete)

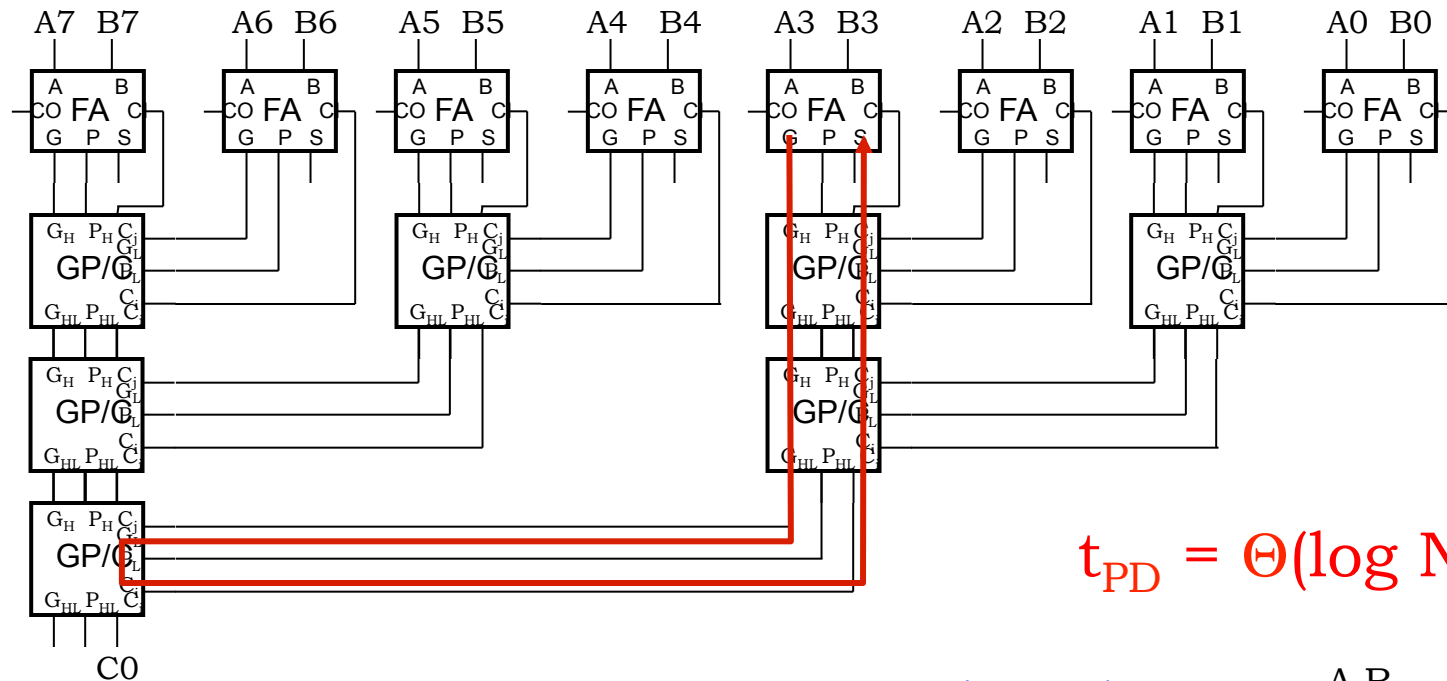


$$t_{PD} = \Theta(\log N)$$

 

To learn more, look up Kogge-Stone adders on Wikipedia.

 Notice that we don't need the carry-out output of the adder any more.





# Binary Multiplication\*

The “Binary”  
Multiplication  
Table

*	0	1
0	0	0
1	0	1

Hey, that  
looks like  
an AND  
gate



\* Actually unsigned binary multiplication

$$\begin{array}{r} A_3 \quad A_2 \quad A_1 \quad A_0 \\ \times B_3 \quad B_2 \quad B_1 \quad B_0 \\ \hline \end{array}$$


$AB_i$  called a “partial product”  $\longrightarrow$

$$\begin{array}{r} A_3B_0 \quad A_2B_0 \quad A_1B_0 \quad A_0B_0 \\ A_3B_1 \quad A_2B_1 \quad A_1B_1 \quad A_0B_1 \\ A_3B_2 \quad A_2B_2 \quad A_1B_2 \quad A_0B_2 \\ + \quad A_3B_3 \quad A_2B_3 \quad A_1B_3 \quad A_0B_3 \\ \hline \end{array}$$

Multiplying N-digit number by M-digit number gives (N+M)-digit result

Easy part: forming partial products (just an AND gate since  $B_i$  is either 0 or 1)  
Hard part: adding M N-bit partial products

# Combinational Multiplier

 

Latency =  $\Theta(N)$   
 Throughput =  $\Theta(1/N)$   
 Hardware =  $\Theta(N^2)$

# 2's Complement Multiplication

Step 1: two's complement operands so high order bit is  $-2^{N-1}$ . Must sign extend partial products and **subtract** the last one

$$\begin{array}{r}
 \begin{array}{cccc} & \text{x3} & \text{x2} & \text{x1} & \text{x0} \\ * & \text{y3} & \text{y2} & \text{y1} & \text{y0} \\ \hline \end{array} \\
 \begin{array}{cccccccc} \text{x3y0} & \text{x3y0} & \text{x3y0} & \text{x3y0} & \text{x3y0} & \text{x2y0} & \text{x1y0} & \text{x0y0} \\ + & \text{x3y1} & \text{x3y1} & \text{x3y1} & \text{x3y1} & \text{x2y1} & \text{x1y1} & \text{x0y1} \\ + & \text{x3y2} & \text{x3y2} & \text{x3y2} & \text{x2y2} & \text{x1y2} & \text{x0y2} & \\ - & \text{x3y3} & \text{x3y3} & \text{x2y3} & \text{x1y3} & \text{x0y3} & & \end{array} \\
 \hline
 \begin{array}{cccccccc} \text{z7} & \text{z6} & \text{z5} & \text{z4} & \text{z3} & \text{z2} & \text{z1} & \text{z0} \end{array}
 \end{array}$$

Step 2: don't want all those extra additions, so add a carefully chosen constant, remembering to subtract it at the end. Convert subtraction into add of (complement + 1).

$$\begin{array}{r}
 \begin{array}{cccccccc} \text{x3y0} & \text{x3y0} & \text{x3y0} & \text{x3y0} & \text{x3y0} & \text{x2y0} & \text{x1y0} & \text{x0y0} \\ + & & & & & & & \text{1} \\ + & \text{x3y1} & \text{x3y1} & \text{x3y1} & \text{x3y1} & \text{x2y1} & \text{x1y1} & \text{x0y1} \\ + & & & & & & & \text{1} \\ + & \text{x3y2} & \text{x3y2} & \text{x3y2} & \text{x2y2} & \text{x1y2} & \text{x0y2} & \\ + & & & & & & & \text{1} \\ + & \text{x3y3} & \text{x3y3} & \text{x2y3} & \text{x1y3} & \text{x0y3} & & \end{array} \\
 \left. \begin{array}{c} \\ \\ \\ \\ \end{array} \right\} -B = \sim B + 1 \\
 \begin{array}{cccccccc} & & & & & & & \text{1} \\ + & & & & & & & \text{1} \\ + & & \text{1} & & & & & \text{1} \\ - & & \text{1} & \text{1} & \text{1} & \text{1} & & \end{array}
 \end{array}$$

Step 3: add the ones to the partial products and propagate the carries. All the sign extension bits go away!


$$\begin{array}{r}
 \begin{array}{cccc} & & & \text{x3y0} & \text{x2y0} & \text{x1y0} & \text{x0y0} \\ + & & & \text{x3y1} & \text{x2y1} & \text{x1y1} & \text{x0y1} \\ + & & \text{x3y2} & \text{x2y2} & \text{x1y2} & \text{x0y2} & \\ + & \text{x3y3} & \text{x2y3} & \text{x1y3} & \text{x0y3} & & \\ + & & & & & & \text{1} \\ - & & \text{1} & \text{1} & \text{1} & \text{1} & \end{array}
 \end{array}$$

Step 4: finish computing the constants...

$$\begin{array}{r}
 \begin{array}{cccc} & & & \text{x3y0} & \text{x2y0} & \text{x1y0} & \text{x0y0} \\ + & & & \text{x3y1} & \text{x2y1} & \text{x1y1} & \text{x0y1} \\ + & & \text{x3y2} & \text{x2y2} & \text{x1y2} & \text{x0y2} & \\ + & \text{x3y3} & \text{x2y3} & \text{x1y3} & \text{x0y3} & & \\ + & \text{1} & & & & & \text{1} \end{array}
 \end{array}$$

Result: multiplying 2's complement operands takes just about same amount of hardware as multiplying unsigned operands!


# 2's Complement Multiplier

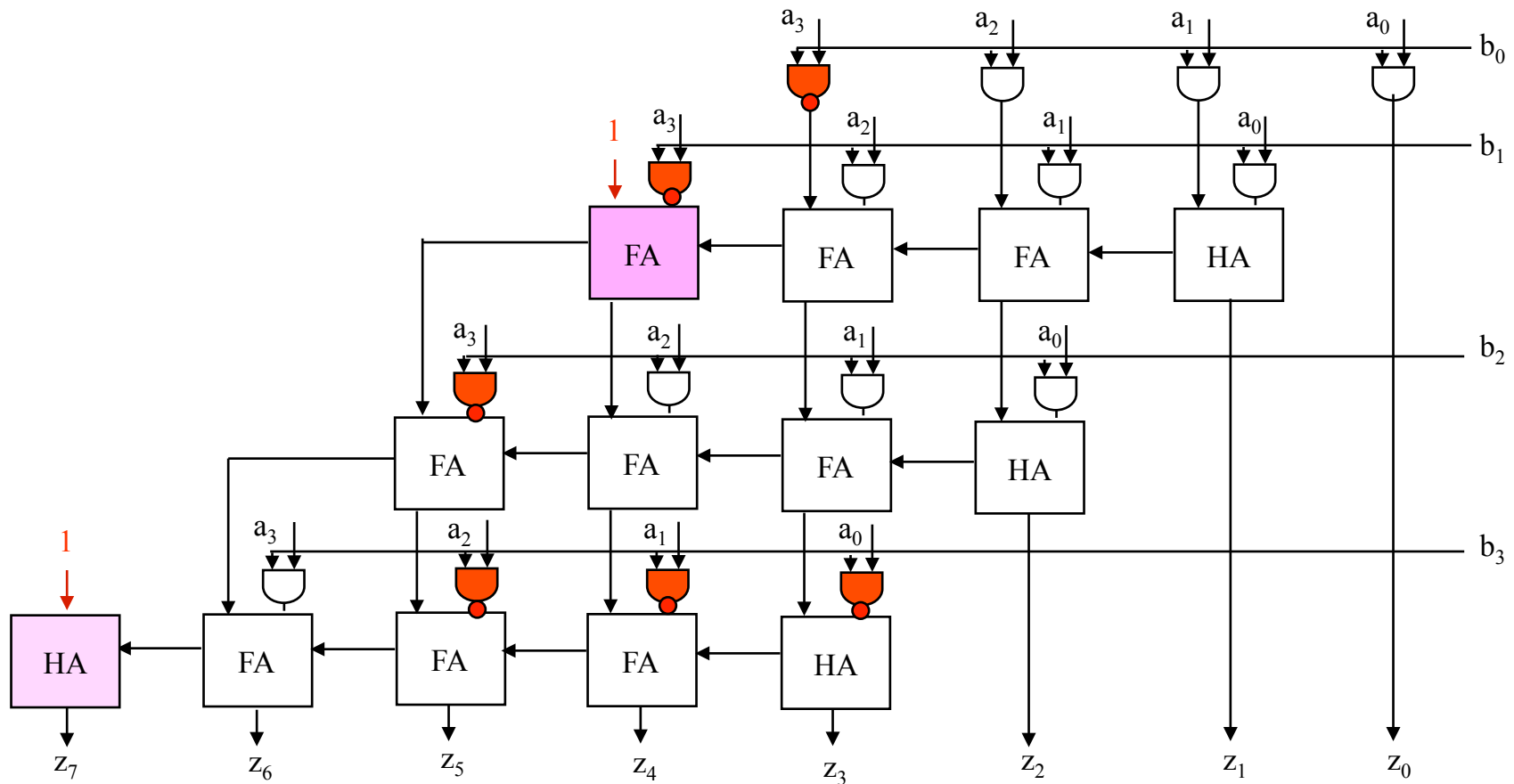





# Increase Throughput With Pipelining

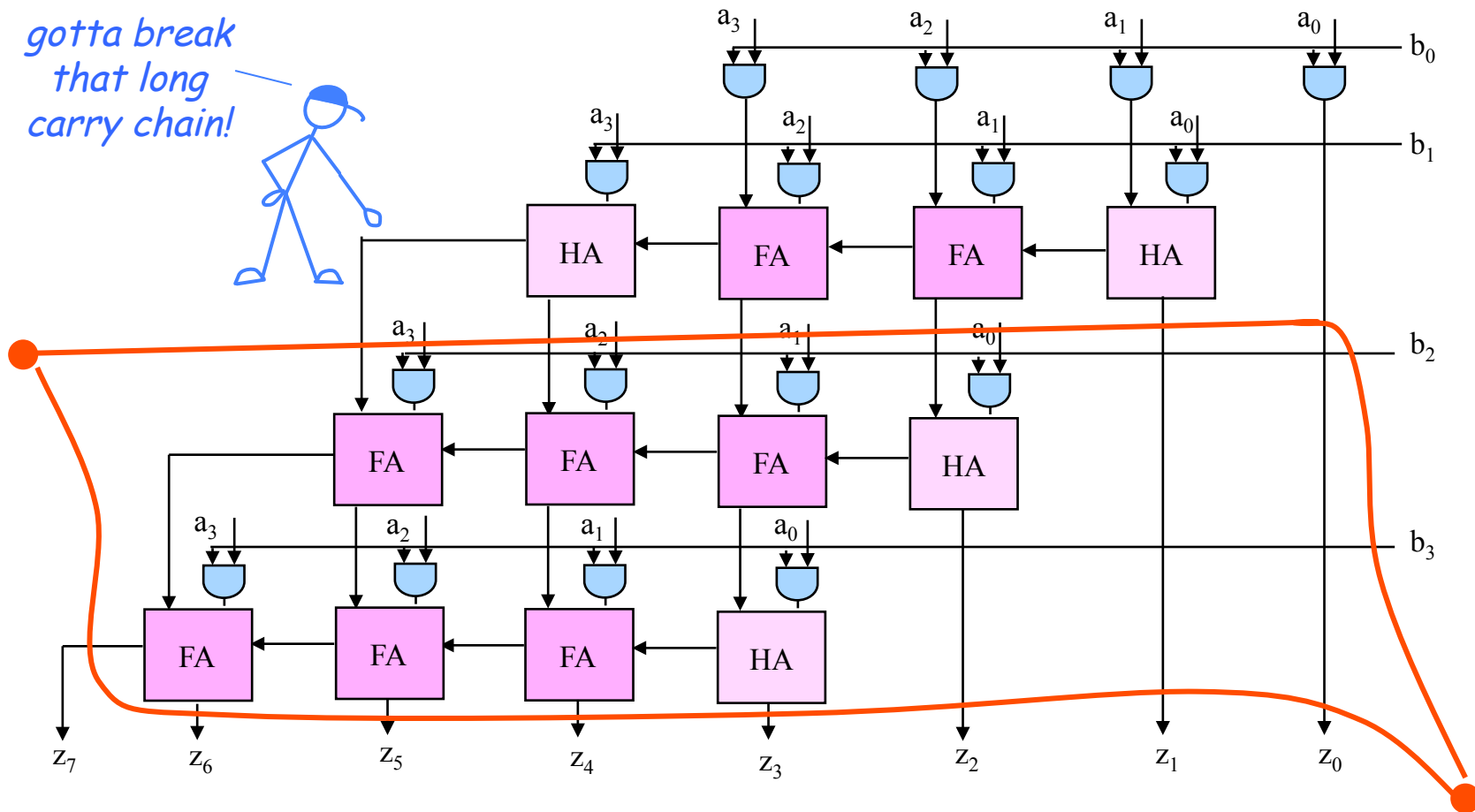


Before pipelining: Throughput =  $\sim 1/(2N) = \Theta(1/N)$

After pipelining: Throughput =  $\sim 1/N = \Theta(1/N)$

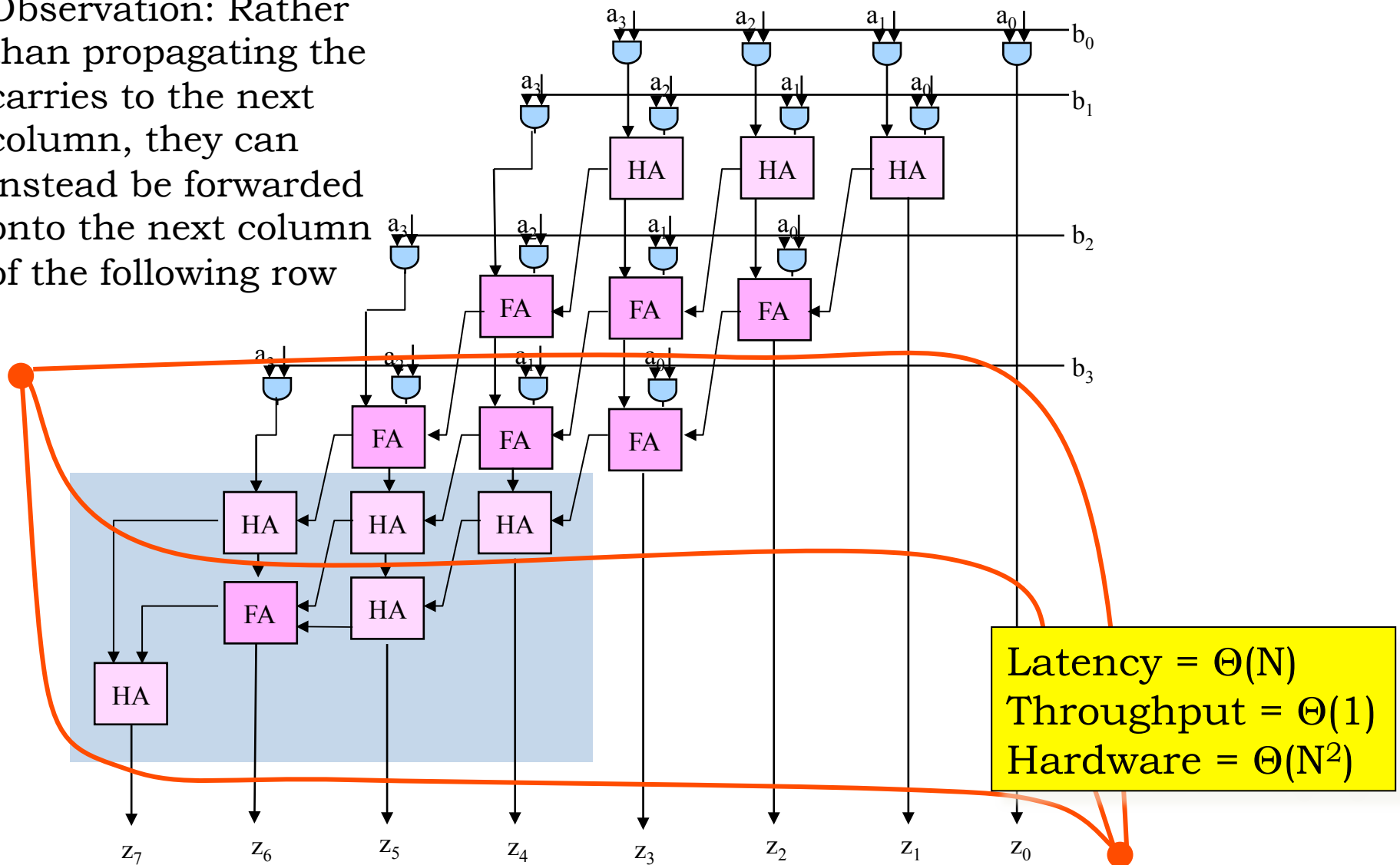
# “Carry-save” Pipelined Multiplier

Observation: Rather than propagating the carries to the next column, they can instead be forwarded onto the next column of the following row


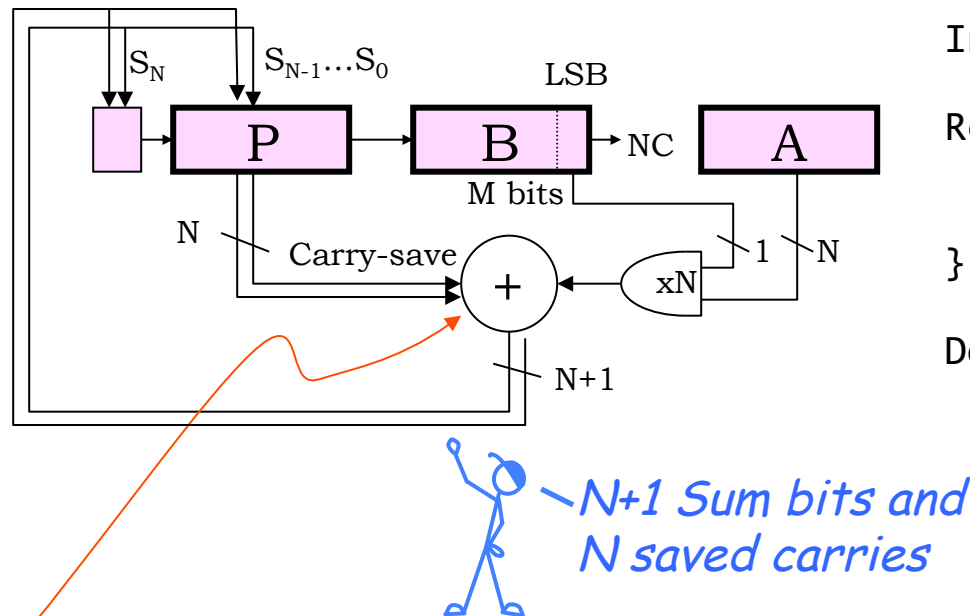
# Reduce Area With Sequential Logic

Assume the multiplicand (A) has N bits and the multiplier (B) has M bits. If we only want to invest in a single N-bit adder, we can build a sequential circuit that *processes a single partial product at a time* and then cycle the circuit M times:



Init:  $P \leftarrow 0$ , load A&B

Repeat M times {  
 $P \leftarrow P + (B_{\text{LSB}} == 1 ? A : 0)$   
 shift  $S_N, P, B$  right one bit  
}

Done: (N+M)-bit result in P,B

Latency =  $\Theta(N)$   
 Throughput =  $\Theta(1/N)$   
 Hardware =  $\Theta(N)$

$T_{PD} = \Theta(1)$  for carry-save (see previous slide),  
 but adds  $\Theta(N)$  cycles &  $\Theta(N)$  hardware

# Summary

- Power dissipation can be controlled by dynamically varying  $T_{CLK}$ ,  $V_{DD}$  or by selectively eliminating unnecessary transitions.
- Functions with  $N$  inputs have minimum latency of  $O(\log N)$  if output depends on all the inputs. But it can take some doing to find an implementation that achieves this bound.
- Performing operations in “slices” is a good way to reduce hardware costs (but latency increases)
- Pipelining can increase throughput (but latency increases)
- Asymptotic analysis only gets you so far – factors of 10 matter in real life and typically  $N$  isn't a parameter that's changing within a given design.